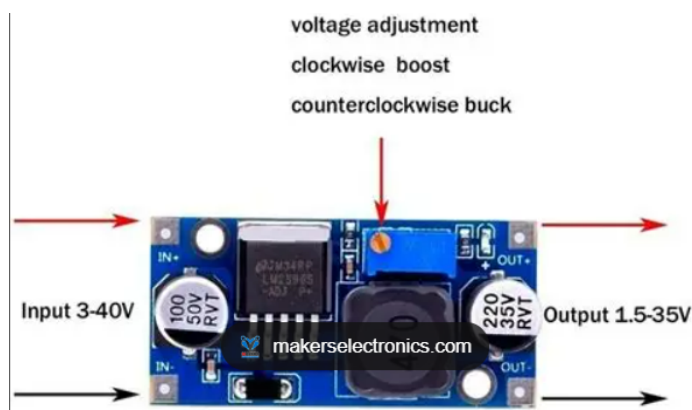


EsiBot Wiring

Component 1 — (3× 18650, 3.7V, 2000mAh) 3S


Pin	Connects to	Component	Notes
(+) positive	VIN	LM2596 DC-DC converter	Raw ~11.1v input to converter
(+) positive	VSS	L298N	Raw ~11.1V direct to motor supply — do NOT regulate
(-) negative	Common GND rail	—	Star point for all grounds

Component 2 — LM2596 DC-DC step-up converter




Pin	Connects to	Component	Notes
VIN	(+) positive	3s battery	Receives raw ~11.1V
GND (input)	Common GND rail	—	—
VOUT	VCC (5V input)	ESP32-CAM	Regulated 5V — set with multimeter before connecting
VOUT	VCC logic supply	L298N motor driver	Logic supply only, separate from VSS
VOUT	VCC (red wire)	MG996R servo	MG996R draws up to 2.5A stall — factor into total current budget
VOUT	VCC	HC-SR04 sensor	Sensor runs on 5V
GND (output)	Common GND rail	—	Input and output GND both go to common rail

Component 3 — ESP32-CAM (AI-Thinker)

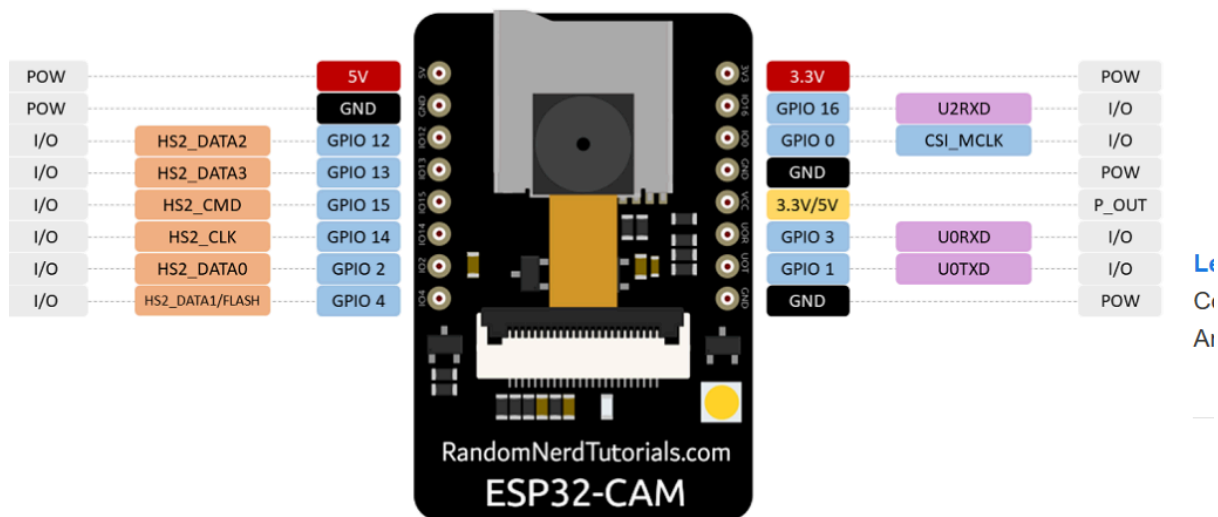

Pin	Connects to	Component	Notes
VCC (5V)	VOUT	LM2596	5V regulated supply
GND	Common GND rail	—	Must share common ground with RPi for UART to work
GPIO1 (U0TXD)	GPIO15 / RXD (Pin 10)	Raspberry Pi 4	UART TX — ESP32 sends camera data to RPi
GPIO3 (U0RXD)	GPIO14 / TXD (Pin 8)	Raspberry Pi 4	UART RX — ESP32 receives commands from RPi

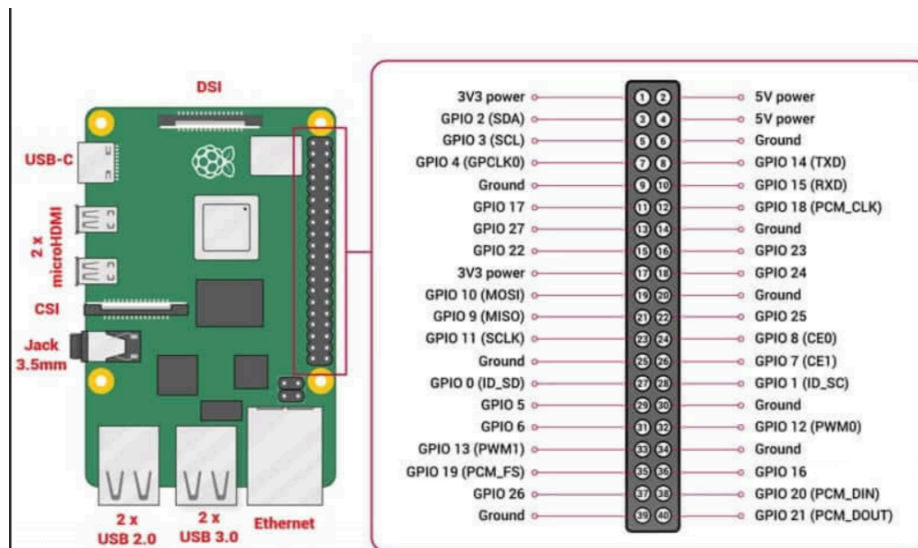
Component 4 — Raspberry Pi 4 (Model B, 8GB) alimentated with powerbank



Updated Full RPi GPIO Map (Component 4)

RPi Pin	GPIO	Connects to	Component	Notes
Pin 1	3.3V	VCC	Both wheel encoders	3.3V supply
Pin 6	GND	Common GND rail	—	Must share common ground with ESP32
Pin 8	GPIO14 TXD	GPIO3 / U0RXD	ESP32-CAM	UART TX → ESP32
Pin 10	GPIO15 RXD	GPIO1 / U0TXD	ESP32-CAM	UART RX ← ESP32
Pin 11	GPIO17	OUT	Left wheel encoder	✓ Interrupt capable — odometry left
Pin 12	GPIO18	ENA	L298N	✓ Hardware PWM — Left motor speed
Pin 16	GPIO23	TRIG	HC-SR04	3.3V output is enough ✓
Pin 18	GPIO24	OUT	Right wheel encoder	✓ Interrupt capable ← moved from Pin 12
Pin 22	GPIO25	ECHO (via divider)	HC-SR04	⚠ Never direct — divider mandatory ← moved from Pin 18
Pin 29	GPIO5	IN1	L298N	Left motor direction


Pin 31	GPIO6	IN2	L298N	Left motor direction
Pin 32	GPIO12	Signal (orange wire)	MG996R servo	⚠ Hardware PWM — 1kΩ series resistor
Pin 33	GPIO13	IN3	L298N	Right motor direction ✓ unchanged
Pin 35	GPIO19	ENB	L298N	✓ Hardware PWM — Right motor speed
Pin 37	GPIO26	IN4	L298N	Right motor direction ← moved from Pin 35

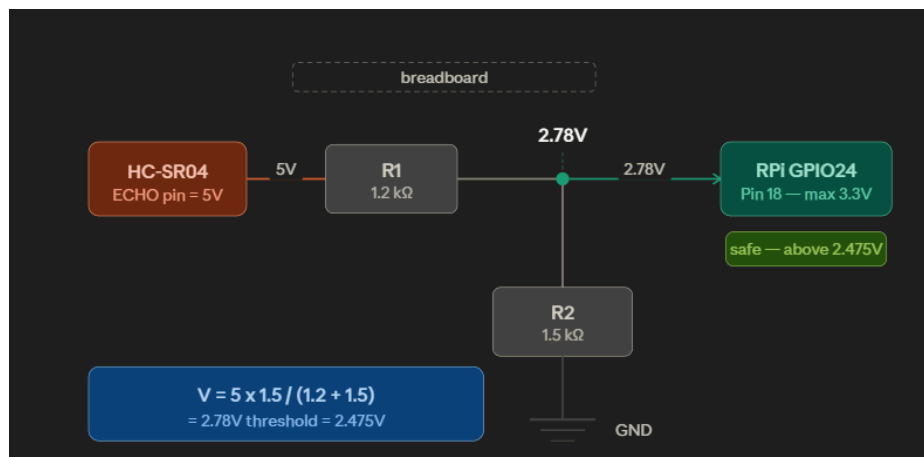

Voltage divider: R1 = 1.2kΩ between ECHO and RPi GPIO25 (Pin 22). R2 = 1.5kΩ between RPi GPIO25 (Pin 22) and GND — Resulting voltage = $5 \times 1.5 / (1.2 + 1.5) = 2.78V$

Node	Connects to	Notes
R1 (1.2kΩ) pin 1	HC-SR04 ECHO	Receives 5V from sensor
R1 (1.2kΩ) pin 2	RPi GPIO25 (Pin 22) AND R2 pin 1	Junction point — 2.78V here ✓
R2 (1.5kΩ) pin 1	R1 pin 2 AND RPi GPIO25 (Pin 22)	Same junction
R2 (1.5kΩ) pin 2	Common GND rail	—

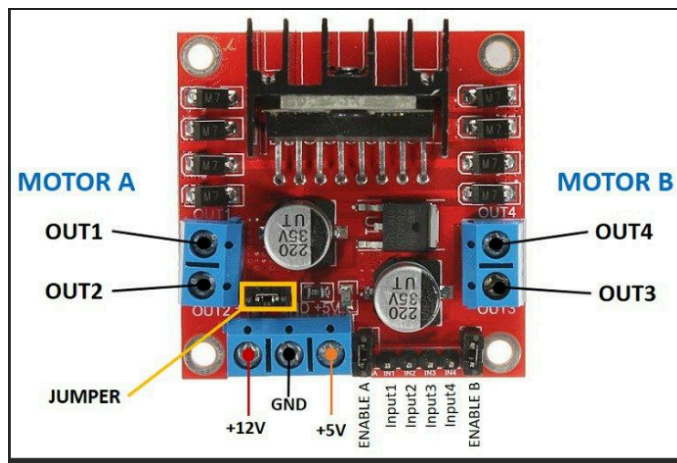Component 5 — L298N dual H-bridge motor driver



Pin	Connects to	Component	Notes
VSS	(+) positive	LiPo 3S battery	Raw ~11.1V — direct, NOT regulated
VCC	VOUT	LM2596	5V logic supply
GND	Common GND rail	—	—
ENA	GPIO18 (Pin 12)	Raspberry Pi 4	✓ Hardware PWM — remove 5V bridge wire
ENB	GPIO19 (Pin 35)	Raspberry Pi 4	✓ Hardware PWM — remove 5V bridge wire
IN1	GPIO5 (Pin 29)	Raspberry Pi 4	Left motor direction
IN2	GPIO6 (Pin 31)	Raspberry Pi 4	Left motor direction
IN3	GPIO13 (Pin 33)	Raspberry Pi 4	Right motor direction
IN4	GPIO26 (Pin 37)	Raspberry Pi 4	Right motor direction ← moved
OUT1	Terminal A	Left DC motor	—

OUT2	Terminal B	Left DC motor	—
OUT3	Terminal A	Right DC motor	—
OUT4	Terminal B	Right DC motor	—

Component 6 — Left DC motor (yellow N20)




Pin	Connects to	Component	Notes
Terminal A	OUT1	L298N	—
Terminal B	OUT2	L298N	Swap A and B if motor spins in wrong direction

Component 7 — Right DC motor (yellow N20)


Pin	Connects to	Component	Notes
Terminal A	OUT3	L298N	—
Terminal B	OUT4	L298N	Swap A and B if motor spins in wrong direction

Component 8 — MG996R servo motor

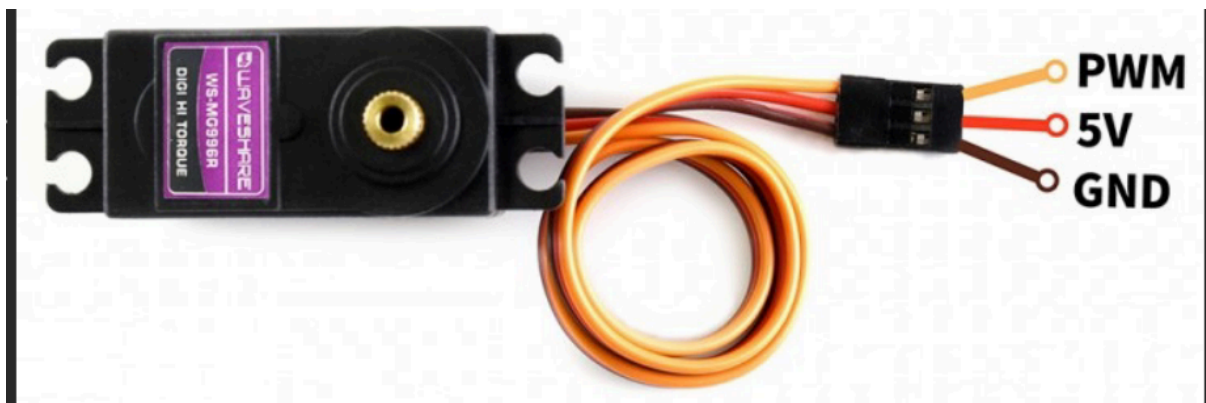

Wire	Connects From	Through	Connects To	Notes
Signal (orange)	RPi Pin 32 (GPIO12)	1k Ω series resistor	MG996R Signal pin	⚠ Hardware PWM mandatory — no other RPi pin works for servo. 1kΩ resistor in series protects GPIO12
VCC (red)	LM2596 VOUT	—	MG996R VCC	5V supply — never from RPi 3.3V pin, draws too much current
GND (brown/black)	Common GND rail	—	MG996R GND	—

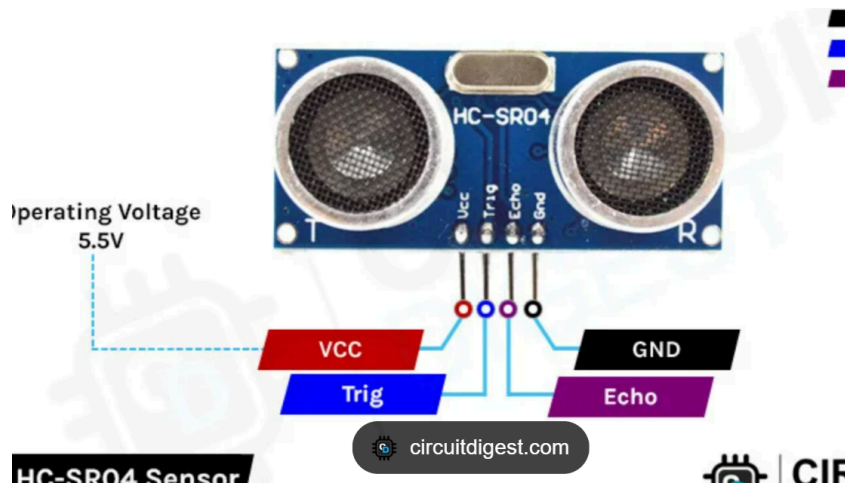Component 9 — HC-SR04 ultrasonic sensor v2.0




The ECHO pin outputs 5V logic which will destroy the ESP32 GPIO (max 3.3V) if connected directly. A voltage divider is mandatory.

Voltage divider: R1 = 1kΩ between ECHO and ESP32-CAM GPIO18. R2 = 2kΩ between ESP32-CAM GPIO18 and GND **Resulting voltage = $5 \times 2/(1+2) = 3.33V$ ✓**

Pin	Connects to	Component	Notes
VCC	VOUT	LM2596	5V supply
GND	Common GND rail	—	—
TRIG	GPIO23 (Pin 16)	Raspberry Pi 4	RPi drives TRIG directly — 3.3V output is enough ✓
ECHO	R1 (1.2kΩ) pin 1	Voltage divider	⚠ Never connect directly to RPi — 5V will damage GPIO , pi in output of divider

Component 10 — Left Wheel Encoder

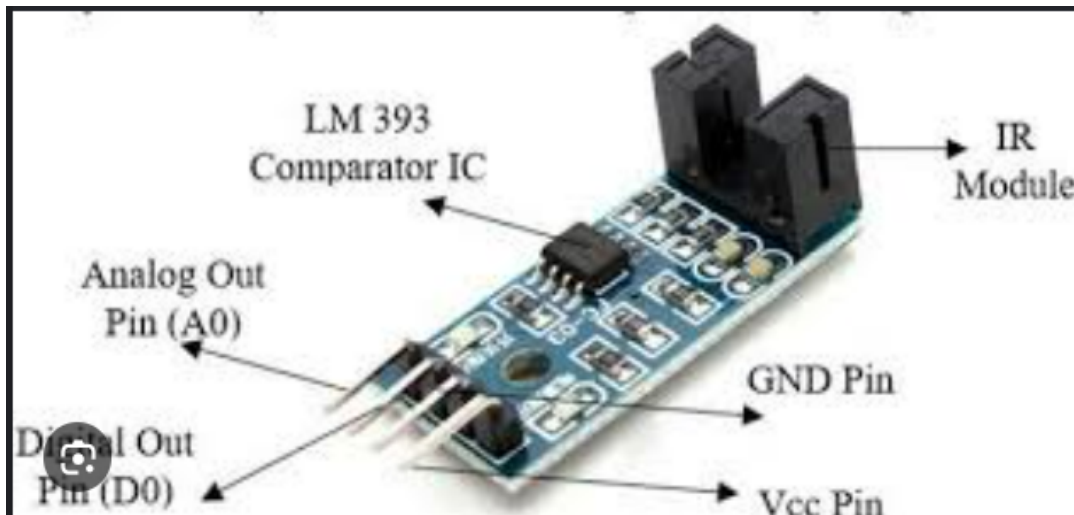

Pin	Connects to	Component	Notes
VCC	Pin 1 (3.3V)	Raspberry Pi 4	3.3V supply — ensures signal level is RPi-safe
GND	Common GND rail	—	—
D0	GPIO17 (Pin 11)	Raspberry Pi 4	✓ Interrupt capable — left wheel odometry

A0 leave empty

Component 11 — Right Wheel Encoder

Pin	Connects to	Component	Notes
VCC	Pin 1 (3.3V)	Raspberry Pi 4	3.3V supply
GND	Common GND rail	—	—
D0	GPIO24 (Pin 18)	Raspberry Pi 4	✓ Interrupt capable ← moved from GPIO18